

ASSIGNMENT 3

Prepare a programmable controller ladder diagram for a motor with the following: NO START button, NC STOP button, thermal overload limit switch opens on high temperature, GREEN light when running, and RED light for thermal overload.